

Chapter 3

COMBINATIONAL CIRCUITS *LARGE DESIGNS*

In this Chapter

- **Design methodologies for large combinational circuits**
 - **Bit-parallel**
 - **Bit-serial**
- **Integer arithmetic as examples**
 - **Add, subtract, multiply, and divide as four basic arithmetic operations**
- **Carry Propagate Adder**
 - **A bit-serial adder**

Top-Down Design Methodology

- **Bit-parallel**

- Partition n -bit design problem into smaller n -bit design problems
- E.g., 8-bit ALU designed using 8-bit adder/subtractor and 8-bit bit-wise logic

- **Bit-serial**

- Partition n -bit design problem into a fewer-bit design problem (called slice)
- E.g., 8-bit ALU designed using eight 1-bit ALU modules

- **Hybrid**

- Design uses bit-parallel and bit-serial modules

Carry Propagate Adder (A bit-serial adder)

- Use FA slices (key Design Aspects)
- Carry bits generated sequentially, one at a time
- Propagation delay proportional to number of carry bits
- Assuming SOP expressions for sum and carry bits and 0.1 ns delay for NANDs determine:
 - $\Delta\text{CPA}(8)$
 - $\Delta\text{CPA}(32)$
- CPA is the slowest

$$\Delta\text{CPA}(8) = 1.7 \text{ ns}$$

$$\Delta\text{CPA}(32) = 6.5 \text{ ns, too slow}$$

Carry Look-Ahead (CLA) Adder

- Goal: Generate carry bits in parallel
- Let's examine FA expressions
 - Easy to generate p and g bits in parallel
 - Carry bits are dependent, but can substitute carry expressions to break dependency
 - Once carry bits are known, easy to generate sum bits in parallel
 - $\Delta\text{CLA}(8) = ?$

0.8 ns

FA expression from Ch2:

$$s_i = a_i \oplus b_i \oplus c_{i-1}$$

$$c_i = (a_i \oplus b_i)c_{i-1} + a_i b_i$$

Let,

$$p_i = a_i \oplus b_i$$

$$g_i = a_i b_i$$

$$s_i = p_i \oplus c_{i-1}$$

$$c_i = g_i + p_i c_{i-1}$$

Observations


- If keep substituting previous carry expression in next carry expression will run into Fan-in and fan-out problems
- **Solution:** Generate some carry bits sequentially and some in parallel (next slide)

Large CLA Adder

1. Group carry bits into equal sized sets with sets resulting in no fan-in or fan-out problem
2. Generate carry bits in two steps
 - What is the longest signal path from inputs to outputs?
 - Determine $\Delta\text{CLA}(32)$

$$\Delta\text{CLA}(32) = 1.2 \text{ ns}$$

Example: For simplicity assume $n = 8$

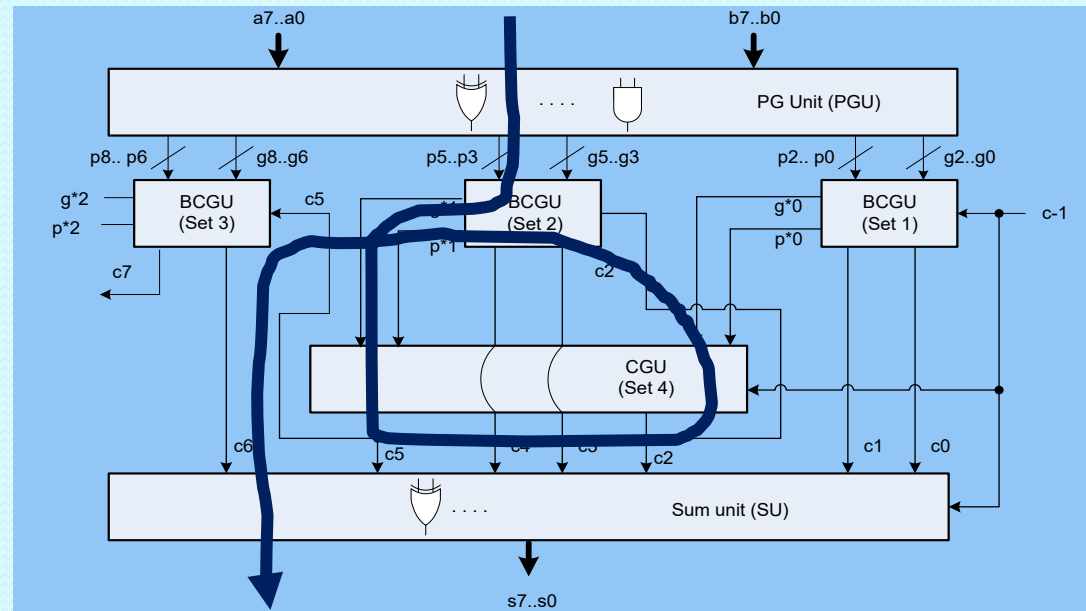

Subtractor

- Similar expressions as FA:

$$d_i = x_i \oplus y_i \oplus b_{i-1}$$

$$b_i = (\overline{x_i \oplus y_i})b_{i-1} + \bar{x}_i y_i$$

- Can use adder to do subtraction if both are needed
 - 2's complement adder/subtractor

| | |
|--|--|
| $ \begin{array}{r} \dots b_i \leftarrow b_{i-1} \leftarrow \dots \\ \dots \quad \quad \quad x_i \quad \quad \dots \\ - \quad \dots \quad \quad y_i \quad \dots \\ \hline \dots \quad \quad d_i \quad \dots \end{array} $ | $ \begin{array}{r} \dots 0 \leftarrow 1 \leftarrow \dots \\ \dots \quad \quad \quad 0 \quad \quad \dots \\ - \quad \dots \quad \quad 1 \quad \dots \\ \hline \dots \quad \quad 0 \quad \dots \end{array} $ |
|--|--|

Twos Complement Adder/Subtractor


- $A - B$ can be viewed as adding A with $-B$
- Circuits for $A + B$ and $A + (-B)$ are similar except second input is negated when subtracting
- What do we know about converting negative numbers to 2's complement representation?
 1. Flip bits
 - Can be done with NOT gates
 2. Add 1
- Addition:
 - Do not flip B bits
 - Set carry-in to 0
 - Carry-out not part of the result
- Subtraction:
 - Flip B bits
 - Set carry-in to 1
 - Carry-out not part of the result
- How to combine into one circuit? Use a control bit m for mode.
 - Add when $m = 0$
 - Subtract when $m = 1$
 - Need an inverter circuit controlled by m
- Potential problem?
 - Result can overflow and become incorrect
 - Need overflow detection logic

Arithmetic Overflow

- **When sum of two positive numbers is negative**
 - I.e., Sign of result becomes 1
 - Applies to subtraction too
 - $A - B$ when $A > 0$ and $B < 0$
- **When sum of two negative numbers is positive**
 - Sign of result becomes 0
 - Applies to subtraction too
 - $A - B$ when $A < 0$ and $B > 0$
- **A simple rule to detect overflow**
 - **Overflow when carry-in to sign bit position \neq carry-out from sign bit position**

Arithmetic Logic Unit (ALU)

 - **Performs arithmetic or bit-wise logic functions**
 - **A function code specifies which operation to perform**
 - **A complex combinational circuit**
- **Need to use bit-parallel or bit-serial design methodology**
- **Overflow flag (OVF) can only be active when performing arithmetic operations**
 - **Must be masked otherwise**




Example

| f2 | f1 | f0 | Function |
|----|----|----|-------------|
| 0 | 0 | 0 | Add |
| 0 | 0 | 1 | Sub |
| 0 | 1 | 0 | Increment |
| 0 | 1 | 1 | Decrement |
| 1 | 0 | 0 | Bitwise AND |
| 1 | 0 | 1 | Bitwise OR |
| 1 | 1 | 0 | Bitwise NOT |
| 1 | 1 | 1 | Not Defined |

ALU Bit-Parallel Design

- Identify different types of operations
 - n-bit Arithmetic**
 - Add, subtract, increment, decrement
 - Can combine into one 2's complement adder/subtractor
 - n-bit Bit-wise operators**
 - NOT, AND, OR
- Assume you have these modules draw a data path
 - Use MUX to select only one output
 - Include other necessary circuits
 - Circuit to convert input F into internal data path signals
 - Circuit to mask OVF during bit-wise operations
- Design modules and assemble

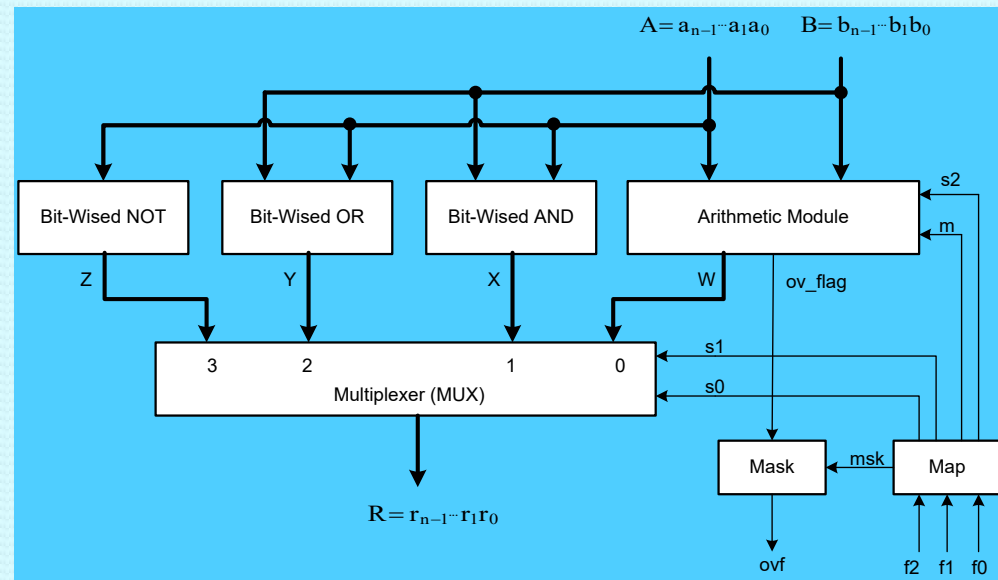

Example ALU Modules

- **Design Arithmetic module**
 - Use n-bit 2's complement adder/subtractor
 - Left input always A
 - Right input either B or 1
 - Need a circuit that outputs B if add/sub or 1 if inc/dec.
 - Use known modules when possible
- **Design n-bit 4-to-1 MUX**
 - Bit-parallel: Design using n-bit 2-to-1 MUXs (bit-parallel)
 - Bit-serial: Design using 1-bit 4-to-1 MUX slices
- **Design Map and Mask circuits**
 - Create truth tables
 - Find minimal SOP/POS expressions

ALU Bit-Serial Design

- Consider n copies of 1-bit ALU slices
 - Create truth table for 1-bit ALU slice
 - Use Espresso
- May use larger slices
 - 2-bit or 4-bit, for example
 - Larger slices may be designed bit-parallel
- Can be slow for large n

| f2 | f1 | f0 | a | b | ci | co | r | Function |
|----|----|----|---|---|----|----|---|---------------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | Add |
| | | | 0 | 0 | 1 | 0 | 1 | |
| | | | 0 | 1 | 0 | 0 | 1 | |
| | | | 0 | 1 | 1 | 1 | 0 | |
| | | | 1 | 0 | 0 | 0 | 1 | |
| | | | 1 | 0 | 1 | 1 | 0 | |
| | | | 1 | 1 | 0 | 1 | 0 | |
| | | | 1 | 1 | 1 | 1 | 1 | |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | Sub |
| | | | 0 | 0 | 1 | 1 | 1 | |
| | | | 0 | 1 | 0 | 1 | 1 | |
| | | | 0 | 1 | 1 | 1 | 0 | |
| | | | 1 | 0 | 0 | 0 | 1 | |
| | | | 1 | 0 | 1 | 0 | 0 | |
| | | | 1 | 1 | 0 | 0 | 0 | |
| | | | 1 | 1 | 1 | 1 | 1 | |
| 0 | 1 | 0 | 0 | d | 1 | 0 | 1 | Increment |
| | | | 1 | d | 0 | 0 | 1 | |
| | | | 1 | d | 1 | 1 | 0 | |
| 0 | 1 | 1 | 0 | d | 1 | 1 | 1 | Decrement |
| | | | 1 | d | 0 | 0 | 1 | |
| 1 | 0 | 0 | 1 | 1 | d | d | 1 | Bit-wised AND |
| 1 | 0 | 1 | 0 | 1 | d | d | 1 | Bit-wised OR |
| | | | 1 | 0 | d | d | 1 | |
| | | | 1 | 1 | d | d | 1 | |
| 1 | 1 | 0 | 0 | d | d | d | 1 | Bit-wised NOT |
| | | | 1 | d | d | d | 0 | |
| 1 | 1 | 1 | d | d | d | d | d | Not Defined |

Truth Table for 1-bit ALU slice

Other design examples (unsigned multiplier)

Algorithm

```

      1 0 0 1  A
    * 1 0 1 1  B
    -----
      1 0 0 1
     0 0 0 0
    + 1 0 0 1
    -----
    1 1 0 0 0 1 1  P = B * A
  
```


- Bit-parallel**

- Addends are added one at a time after adding 1st two
- Less concurrency in the data path
- Slower, longer propagation delay


- Bit-serial**

- Addend bits are added vertically, the way numbers are added by hand
- More concurrency in the data path
- Faster, shorter propagation delay

Bit-parallel

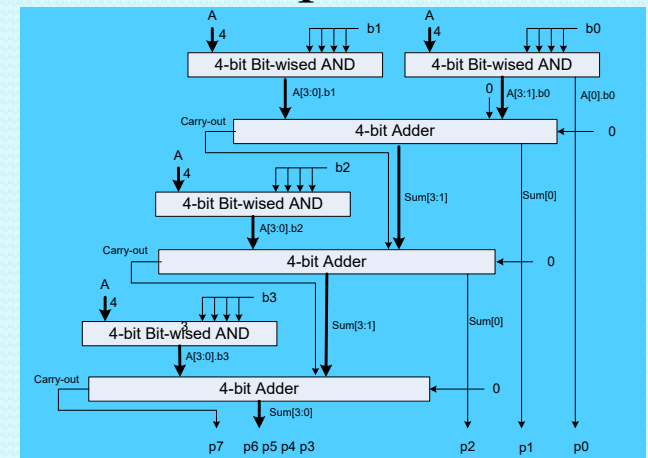


Bit-serial

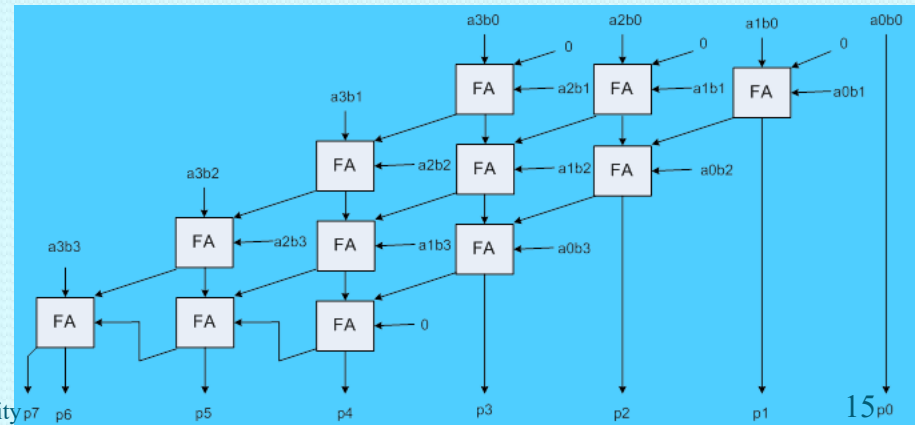

Unsigned Divider (restoring)

- **Similar to how we divide by hand**
 - In each step, remainder can be + or -
 - If remainder positive, use in the next step
 - Else, restore
 - Concatenate next numerator bit and repeat
- **Bit-parallel**
 - Requires subtractor and MUX modules
- **Bit-serial**
 - Can use 1-bit combined subtractor/MUX slices
 - See Exercise section

Bit-parallel

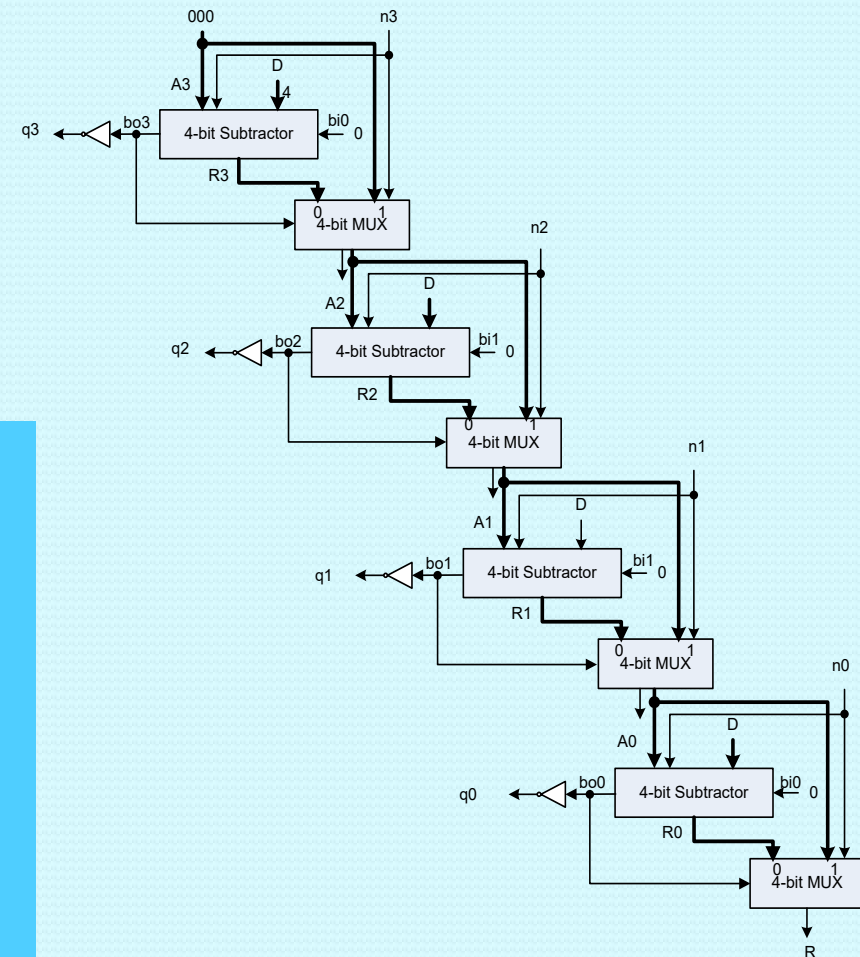

| | | |
|-----------------|---------------|---------------|
| | 0 1 0 1 | Q = q3q2q1q0 |
| D 0 0 1 0 | 0 0 0 1 0 1 1 | N, A3 = 0001 |
| | - 0 0 1 0 | D > A3 |
| q3 = 0 ← bo = 1 | 1 1 1 1 | R3 = 1111 |
| | 0 0 0 1 0 | A2 = 0010 |
| | - 0 0 1 0 | D = A2 |
| q2 = 1 ← bo = 0 | 0 0 0 0 | R2 = 0000 |
| | 0 0 0 0 1 | A1 = 0001 |
| | - 0 0 1 0 | D > A1 |
| q1 = 0 ← bo = 1 | 1 1 1 1 | R1 = 1111 |
| | 0 0 0 1 1 | A0 = 0011 |
| | - 0 0 1 0 | D < A0 |
| q0 = 1 ← bo = 0 | 0 0 0 1 | R = R0 = 0001 |

Real Number Arithmetic

IEEE 754 FP number Standards


- **Single, 32 bits**
 - 1-bit sign, 8-bit biased exponent (bias = 127), 23-bit fraction
 - Stored as a 32-bit number in memory
- **double, 64 bits**
 - 1-bit sign, 11-bit biased exponent (bias = 1023), 52-bit fraction
 - Stored as a 64-bit number in memory
- **Extended, 80 bits**
 - 1-bit sign, 15-bit bias exponent (bias = 16383), 64-bit fraction
 - Stored in 80-bit registers only (no memory representation)

FP number Data Space (assume 32-bit FP numbers)

- **Normal**
 $1 \leq \text{Biased exponent} \leq 254$
- **Denormal**
 - Biased exponent = 0 and fraction $\neq 0$
- **Zero**
 - Biased exponent = 0 and fraction = 0
- **Infinity**
 - Biased exponent = 255 and fraction = 0
 - E.g., $\frac{1}{0}$
- **Not-a-number (Nan)**
 - Biased exponent = 255 and fraction $\neq 0$
 - E.g., $\sqrt{-1}$


Data Space Illustration (1-Dimensional)

 - Bold and thin lines indicate real numbers stored as FP numbers in computer
- More fraction bits implies more thin lines
- More exponent bits implies more bold lines



Two-Dimensional Illustration

 - Easier to identify data space regions
- Easier to mark specific FP numbers or domain or range of a function
 - Eg. The largest FP number
 - E.g., for test generation purposes
 - region identified by $(-1, 1)$ or $[-1, 1]$, for example



FP Arithmetic

- **Requires integer arithmetic**
 - Operates on exponent and fraction numbers independently
 - Typically combinational arithmetic circuits
- **Requires shift operations**
 - Typically combinational shifter circuits
 - Used to line up implicit decimal points
 - **E.g., during FP add**
 - Used for normalizing results
 - **Result converted to standard format**
 - Used for rounding results
 - **64-bit fraction in register is converted to 23 or 52 bits format for storage**
 - “float” data type: 23-bit fraction
 - “double” data type: 52-bit fraction
 - **The resultant fraction is rounded**
 - Based on the value of the bits lost
 - May require another normalization step

FP Add

(e.g., $S = A + B$)

1. Switch operands (if necessary)
 - For $S = A + B$, $|A|$ must be $\geq |B|$
2. Align decimal points and compute result $R.F = A.F + B.F$
3. Normalize $R.F$
4. Round $R.F$ to produce $S.F$
 - Example

FP subtract, multiply, divide

- **Subtraction**
 - Lineup decimal points
 - Compute $A - B$ if $A.s = B.s$ or $A + B$ if $A.s \neq B.s$.
- **Multiplication**
 - Integer multiply fractions
 - Add exponents
 - XOR the sign bits
- **Division**
 - Integer divide fractions
 - Subtract exponents
 - XOR the sign bits
- **The rounding and normalization steps are the same as in FP add**