

Chapter 5

SEQUENTIAL CIRCUITS: *Small Designs*

In this Chapter

- Sequential circuit design models
- Design examples:
 - registers, counters, sequence recognizer
- Sequential circuit timing
- Interfacing sequential circuits

Sequential Circuit as a Finite State Machine (FSM)

- Requires flip-flop(s) to save circuit state
- There are three types of FSMs.
 - Mealy State Machine
 - Moore State Machine
 - Hybrid
- Requires combinational circuit(s) to generate next circuit state and output(s)
- Two types of circuits:
 - Functions of the circuits cannot be determined in advance
 - **FSM design is modeled with a finite state diagram (FSD)**
 - Functions of the circuits can be determined in advance
 - **E.g., MUX, adder, ALU**
 - **No need for an FSD**

A simple design Example (Parallel-load register with enable)

- Assume unknown combinational circuit
 1. Design 1-bit register 1st
 - We have seen D flip-flop with enable in Ch4
 - Here, the flip-flop formally modeled as FSD (next slide)
 2. Combine register slices to create 4-bit register below
 - *enable, clk, _reset* connect to all

 


Fig 5.2

FSM design steps

(1-bit parallel-load register example)

1. Draw FSD and detailed block diagram of 1-bit register slice

 


Fig 5.3

 


Fig 5.4

2. Convert FSD to truth table (also called transition table)

Current State	External Inputs		Next State
q	E	x	d
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

Table 5.1

4. Draw final circuit

 


Fig 5.5

3. Find minimal SOP or POS expression(s) for the output(s)

$$d = \bar{e}q + ex \quad \text{Ah, a MUX!}$$


Circuit shown 1st in Chap. 4.

Some design rules

- **If cannot determine function(s) of combinational circuit(s) in advance:**
 1. **Model FSM as FSD**
 - **May need to design bit-slice 1st**
 2. **Determine number of flip flops**
 3. **Convert the FSD to truth table**
 4. **Find minimal expressions for next state variable(s) and output(s)**
 5. **Draw the complete circuit with flip-flops**
- **Otherwise**
 - **Use bit-serial design with known modules**
 - **Or, bit-parallel design with known modules**

Multi-Function Register

 - Performs one of many functions
- Can be designed bit-serial or bit-parallel
- If cannot determine function(s) of combinational circuit(s) in advance
 - **Model a bit-slice (e.g., 1-bit) as FSD**
- **Otherwise: Oh, I can use a MUX**
 - **Bit-serial: Use 1-bit 4-to-1 MUXs, for example**
 - **Bit-parallel: Use n-bit 4-to-1 MUX**



f1	f0	Action
0	0	Clear (synchronous reset)
0	1	Load X
1	0	Arithmetic shift (shifts right repeating the sign bit)
1	1	Right shift (shifts right entering 0 from left)

Fig 5.6

FSM

(A formal view)

Three types of FSMs:

- **Moore**

- External inputs do not synchronously affect outputs
- Outputs called Moore

- **Mealy**

- External inputs synchronously affect outputs
- Outputs called Mealy

- **Hybrid**

- Generates both Moore and Mealy outputs

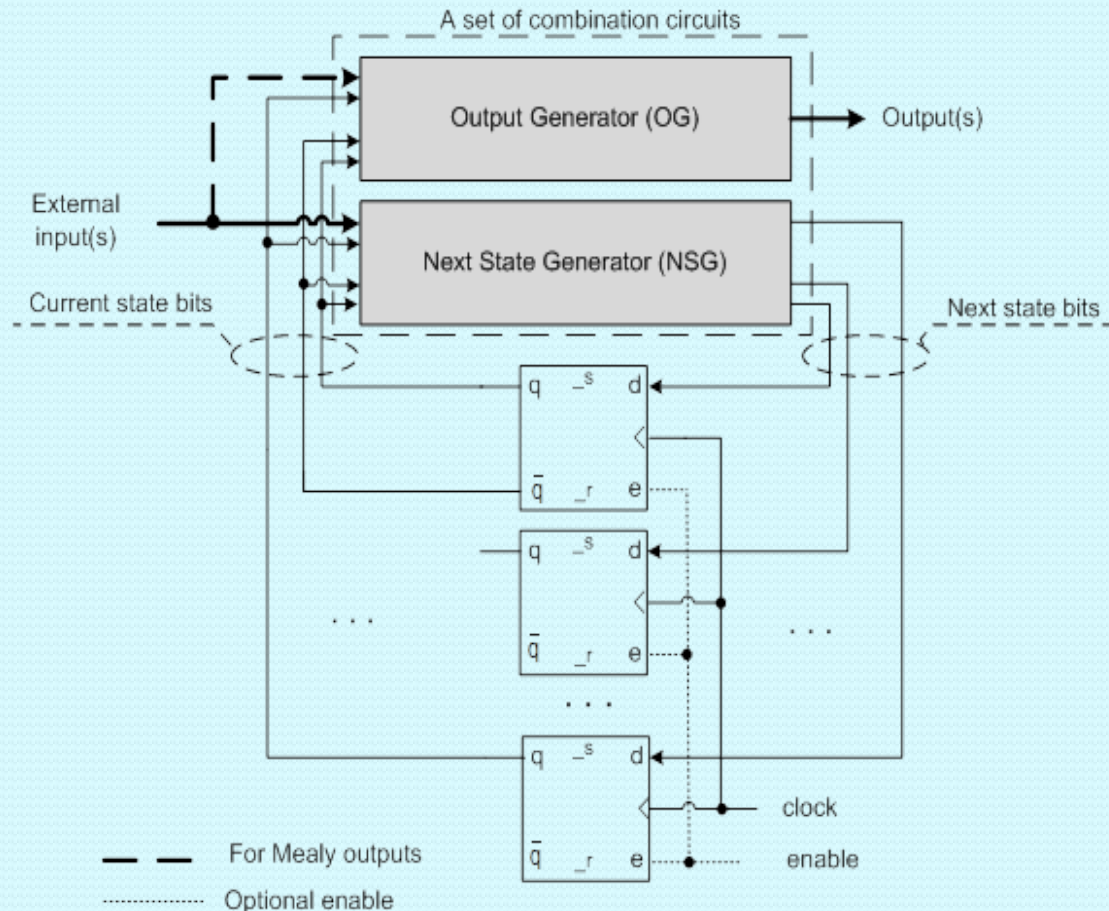



Fig 5.6

Fig 5.12

Sequence Recognizer


Suppose FSM recognizes overlapping input sequence “101”:

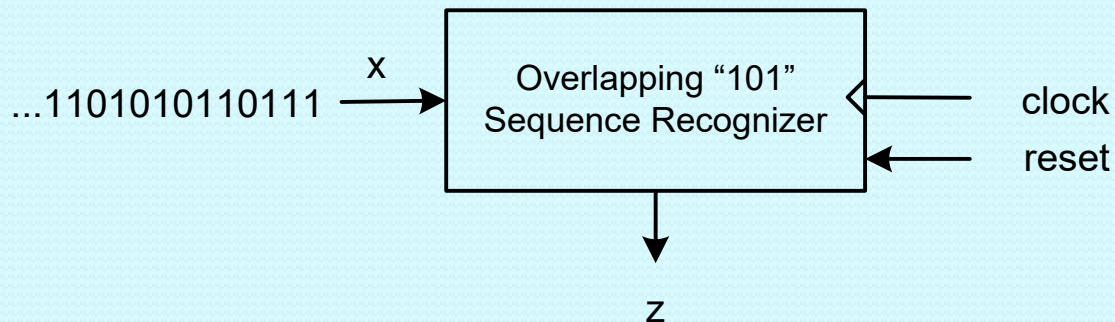- Inputs processed one bit at a time (one per clock cycle)
- Not possible to determine the functions of the combinational circuits in advance
 - Model FSM as FSD
- Reset initializes the machine to known state
- Can be designed either as Moore or Mealy machine



Sequential Circuit Timing (1)


- Clock skew due to delay (τ_{cs}) in clock signal
- Clock skew can create circuit timing problems
 1. If $\Delta cc < \tau_{cs}$, FF2 will load $d2^{New}$ and not $d2^{Current}$
 - FSM results in functional error
 2. If $\Delta cc \sim \tau_{cs}$, $d2$ may be still changing when $clk2$ arrives
 - FSM malfunction due to setup or hold time violation at FF2
- $\Delta cc > \tau_{cs}$, FF2 will load $d2^{Current}$ as it should
 - Circuit will function correctly

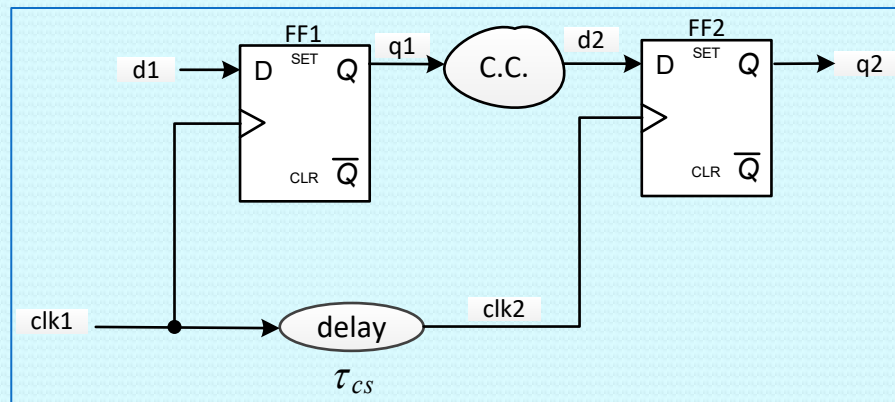

$clk1$ reaches FF1 1st and after some delay
as $clk2$ to FF2

Sequential Circuit Timing (2)

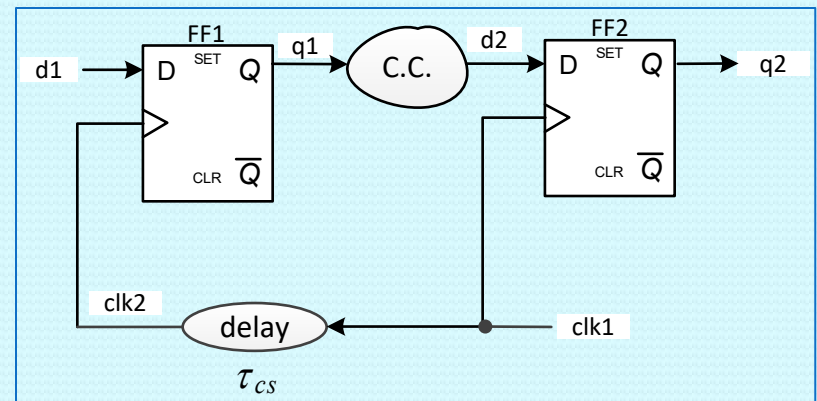- Possible problem: Next *clk1* reaches FF2 before previous *clk2* reaches FF1
 - If $\Delta cc \approx \tau - \tau_{cs}$, *d2* may be still changing when *clk1* arrives
 - FSM malfunction due to setup or hold time violation at FF2
- Normal operation
 - When $\Delta cc < \tau - \tau_{cs}$



clk1 reaches FF2 1st and after some delay
as *clk2* to FF1

Clock Frequency Estimation – With Clock Skew

Add τ_{cs} to the clock period determined in Ch. 4

$$\tau \geq \tau_{cq-max} + \tau_{pd-max} + \tau_{st} + \tau_{cs}$$

Interfacing Sequential Circuits

- **How to handle asynchronous inputs**
 - Asynchronous inputs may change at any time with respect to *clock* signal
 - They can cause setup or hold time violation if directly enter FSM
- **Solution: Use synchronization flip-flop(s)**
 - Asynchronous input d may violate setup or hold time of synchronizing FF, not FFs of FSM
 - q of synchronizing FF will eventually stabilize if setup or hold time violated
 - May use two synchronizing FFs if q slow to stabilize

