

Chapter 2

COMBINATIONAL CIRCUITS *SMALL DESIGNS*

In this Chapter

- **Small Combinational Circuits**
 - Fewer inputs (e.g., ≤ 4 inputs)
 - Circuits modeled as Truth Tables
 - Circuit minimization techniques
- **Circuit implementation options**
 - **NANDs only**
 - **NORs only**
- **Timing diagram**
 - **Signal propagation delay**
 - **Understating signal hazards (“glitches”)**
- **Other types of logic gates**
- **Design examples**

Small Combinational Circuits

- **Example: 2-bit unsigned multiplier, $P = A * B$**
- **Block diagram and truth table**
 - **Labeling of input and output signals**
- **Implementation options**
 - **LUT**
 - **Easier, slower, configurable**
 - **Logic circuit**
 - **Faster, less hardware**


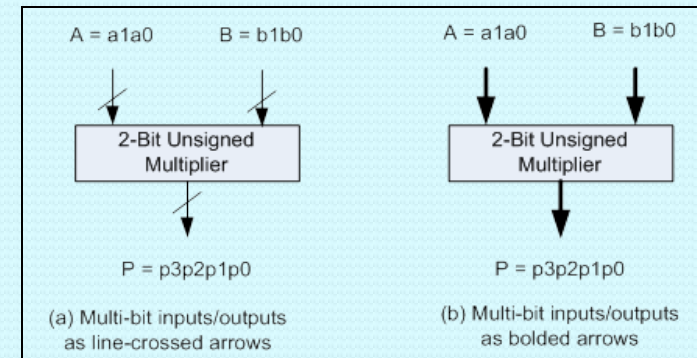


Figure 2.1


Inputs				Outputs			
a1	a0	b1	b0	p3	p2	p1	p0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	1
0	1	1	0	0	0	1	0
0	1	1	1	0	0	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	0	0	0	0
1	1	0	1	0	0	1	1
1	1	1	0	0	1	1	0
1	1	1	1	1	0	0	1

Table 2.1


Logic Gates with Truth Tables

 


x	f
0	1
1	0

 


x	y	f
0	0	0
0	1	0
1	0	0
1	1	1

 

x	y	f
0	0	0
0	1	1
1	0	1
1	1	1

 

x	y	f
0	0	1
0	1	1
1	0	1
1	1	0

 

x	y	f
0	0	1
0	1	0
1	0	0
1	1	0




x	y	f
0	0	0
0	1	1
1	0	1
1	1	0



x	y	f
0	0	1
0	1	0
1	0	0
1	1	1

Signal Naming Standards

 - **Active-high signal polarity**
 - 1 represents signal is active, asserted, enabled
 - 0, otherwise
 - E.g., signal labeled as x without a pre- or post symbol
- **Active-low signal polarity**
 - 0 represents signal is active, asserted, enabled
 - 1, otherwise
 - E.g., signal labeled as $_x$, $/x$, x' , or $x\#$
 - **With a pre- or post-symbol**




$_c$	x	y
0	0	1
0	1	0
1	0	0
1	1	1

SOP Expressions

- Logical expression whose input values produce 1 as output
- Each such input is expressed as a product term
- Circuit performs AND-OR logic

x	y	f
0	0	1
0	1	0
1	0	0
1	1	1

Table 2.3

 

$$f = \bar{x} \bar{y} + x y$$

sum
↓
product


- Can be implemented with NAND gates
- DeMorgan's theorems convert AND-OR circuit into NAND-only circuit

Theorem 1:

$$\overline{xy} = \bar{x} + \bar{y}$$

Theorem 2:

$$\overline{\bar{x} + \bar{y}} = x y$$

 

POS Expressions


- Based on input values that produce 0 for f (an output)
 - Same input values produce 1 for \bar{f}

- Find expression for f by complementing \bar{f}
- Each such input is expressed as a sum term

x	y	f	\bar{f}
0	0	1	0
0	1	0	1
1	0	0	1
1	1	1	0

$$f = (x + \bar{y})(\bar{x} + y)$$

- Circuit performs OR-AND logic

 


- Can be implemented with NOR gates
- De Morgan's theorems convert OR-AND circuit into NOR-only circuit

$$f = (\bar{x}\bar{y})(x\bar{y})$$

- Also can use signal negation with Dual principle
 
$$\text{Dual of } \bar{f} = (\bar{x} + y)(x + \bar{y})$$



Show mathematically

- NAND implementation**

$$f = \bar{\bar{f}} \quad \longrightarrow \quad f = \overline{\bar{x}\bar{y} + xy}$$

Theorem 2

$$\overline{x + y} = \bar{x}\bar{y}$$

$$f = \overline{(\bar{x}\bar{y})(xy)}$$

NAND NAND

NAND, again

- NOR implementation**

$$f = (x + \bar{y})(\bar{x} + y) = \overline{\overline{(x + \bar{y})(\bar{x} + y)}} = \overline{\overline{(x + \bar{y})} + \overline{(\bar{x} + y)}}$$

NOR NOR

NOR, again

Canonical Expression

$$g = \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z + xy\bar{z} + xyz$$

Canonical, every term has all the variable names

$$f = x\bar{y} + \bar{x}z + xyz$$

Non-Canonical

Min Terms vs. Canonical expression

For example, $g(x, y, z) = \sum(0, 1, 6, 7)$

$$g(x, y, z) = \sum((000)_2, (001)_2, (110)_2, (111)_2)$$

$$g = \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z + xy\bar{z} + xyz$$

Inputs				Outputs			
a1	a0	b1	b0	p3	p2	p1	p0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	1
0	1	1	0	0	0	1	0
0	1	1	1	0	0	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
10	1	0	1	0	1	0	0
11	1	0	1	0	1	1	0
	1	1	0	0	0	0	0
	1	1	0	0	0	1	1
14	1	1	1	0	1	1	0
	1	1	1	1	0	0	1

$$p2(a1, a0, b1, b0) = \sum(10, 11, 14)$$

Why minimize logic expressions

- Eliminates redundancies
- Requires fewer gates
- Fewer inputs per gates
- Less wire
- Less power usage
- Reduces circuit delay
- Lowers Manufacturing cost

How many gates and types for SOP?

Canonical SOP:
4 NOTs,
four 3-input ANDs,
one 4-input OR.

Minimal SOP:
One NOT,
two 2-input AND,
one 2-input OR

Implement with NAND gates

Canonical SOP: $f = \bar{x}\bar{y}z + \bar{x}yz + x\bar{y}z + xyz$

Minimal SOP: $f = \bar{x}z + xy$

Implement with NOR gates

Canonical POS: $f = (x + y + z)(x + \bar{y} + z)(\bar{x} + y + z)(\bar{x} + y + \bar{z})$

Minimal POS: $f = (x + z)(\bar{x} + y)$

x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Karnaugh map (K-Map) Layouts

yz:	00	01	11	10
x: 0	0	1	3	2
1	4	5	7	6

2×4

4 × 2		z:	0	1
		xy: 00	0	1
		01	2	3
		11	6	7
		10	4	5

4×2

yz:	00	01	11	10
wx: 00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

4×4

SOP and POS K-maps

yz:	00	01	11	10
x: 0				1
1			1	1

$$g(x, y, z) = \sum(2, 6, 7)$$

SOP

yz:	00	01	11	10
x: 0	0	0	0	
1	0	0		

$$g(x, y, z) = \prod(0, 1, 3, 4, 5)$$

POS

Minimizing SOP Expressions

$$\sum (2,3,6,7) = \bar{x}y\bar{z} + \bar{x}yz + xy\bar{z} + xyz$$

$$= \bar{x}y(\bar{z} + z) + xy(\bar{z} + z) \quad \text{Factor out smaller terms and simplify}$$

$$= \bar{x}y + xy \quad \text{Factor out } y \text{ and simplify}$$

$$= y(\bar{x} + x) \quad \text{Simplify}$$

$$= y$$

yz:	00	01	11	10
x: 0			1	1
1			1	1

Each pair of adjacent terms reduces to a simplified expression with one less variable.

K-Map Minimization Rules

- 1) Min/max terms that differ in only one bit are adjacent (**an Implicant**). A K-map is assumed to wrap around on both sides.
- 2) A set of adjacent min/max terms may be combined to form a large group (**a Prime Implicant**). The number of terms in each group must be powers of 2
e.g., 2, 4, 8, or 16 terms.
- 3) Each group of min/max terms must contain at least a single term that doesn't belong to any other group (no redundant groups), **an Essential Prime Implicant**
- 4) All terms must be grouped.


More K-map Examples (no slides)

Don't-Care Signal values

- Example: Displaying BCD numbers

A 7-segment display unit and converter

Inputs				Outputs						
w	x	y	z	fa	fb	fc	fd	fe	ff	fg
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	0	1	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	1	0	1
0	1	0	1	1	0	1	1	1	0	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	1	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	1	1	1
1	0	1	0							
1	0	1	1							
1	1	0	0							
1	1	0	1							
1	1	1	0							
1	1	1	1							
1	1	1	1							

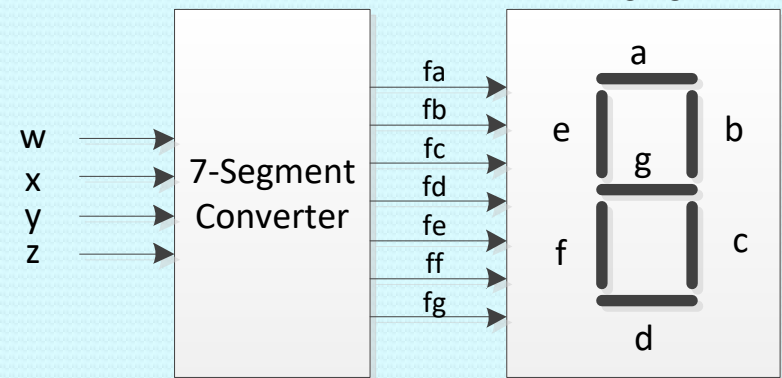

Assuming that w, x, y, and z will not exceed 9, what should we enter in the table for inputs 10 through 15?

K-Map with Don't Cares

$$f(w, x, y, z) = \Sigma(1, 9, 14) + \Sigma_d(3, 7, 11)$$

yz:	00	01	11	10
wx: 00		1	d	
01			d	
11				①
10		1	d	

$$f(w, x, y, z) = \bar{x}z + wxy\bar{z}$$

Logic Minimization Algorithm

- **Based on K-Map minimization technique**
 1. **Compare neighboring min/max terms two at a time (e.g., 0000 with 0001) to produce all Implicants**
 2. **Write the Implicant with a dash (e.g., 000-) for the bit that changes**
 3. **Repeat steps 1 and 2 for neighboring terms with matching dashes (e.g., 000- with 100- to get -00-)**
 4. **Prime implicants: Repeat step 3 until all prime implicants are identified**
 5. **Essential prime implicants: Choose a minimum set among the prime implicants**

Minimization Software

$$f(w, x, y, z) = \Sigma (0, 2, 3, 4, 5, 6, 7, 8, 10, 12, 13)$$

Input File

```
#Inputs: 4, Outputs: 1
.i 4
.o 1
#Input labels
.ilb w x y z
#output bit label
.ob f
#list of min-terms separated by space and a single output bit separated
by a tab
0 0 0 0      1
0 0 1 0      1
0 0 1 1      1
0 1 0 0      1
0 1 0 1      1
0 1 1 0      1
0 1 1 1      1
1 0 0 0      1
1 0 1 0      1
1 1 0 0      1
1 1 0 1      1
#end of list
.e
```



Output

```
#Inputs: 4, Outputs: 1
#Input signal labels
#output bit label
#list of min-terms and output
#end of list
.i 4
.o 1
.ilb w x y z
.ob f
.p 3
-10- 1
-0-0 1
0-1- 1
.e
```



$$\bar{x}\bar{z} + \bar{w}y + x\bar{y}$$


- Can be used with don't care inputs too

Circuit Timing Diagram

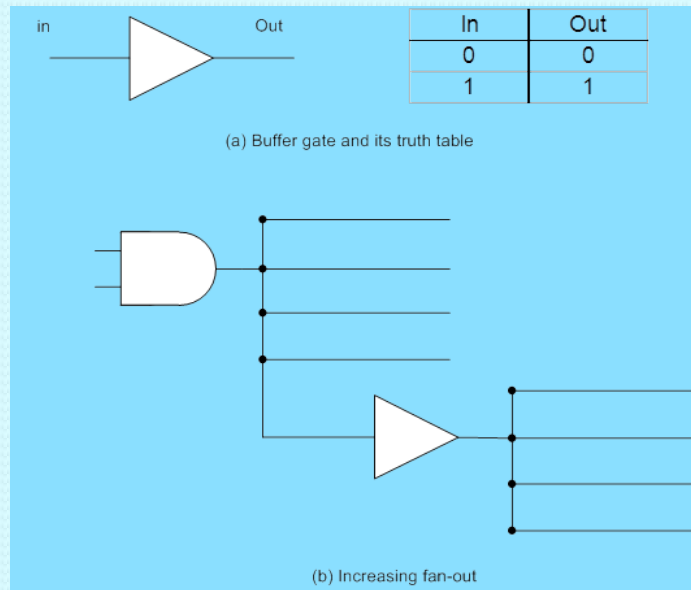1. Circuits have gate and signal wire delays
2. Gates may have different output signal *rise* and *fall* times
3. Circuits have different signal paths from inputs to outputs
 - These may result in signals reaching each gate at different times
 - Can cause unwanted signal change (glitch) at some outputs
 - Must wait for the longest signal propagation delay before the output(s) of a circuit can be used (e.g., stored in a register)


Circuit Fan-In and Fan-Out

- **Fan-in:** Number of gate inputs
- **Fan-out:** Number of places a gate output can connect to
- **Buffer gate to increase a gate's fan-out**



Other Gates

 - **Open collector (o.c.) buffer**
 - **Application: Wired-logic with a large fan-in**
 - **E.g., wired-AND or wired-OR logic**
 - **Many application areas**
- **Tri-state buffer**
 - **Used to create a bus for multiple modules to transmit data**
 - **Modules not outputting to the bus should be electrically isolated**



Small combinational design examples


- **Full-adder circuit**
- **Multiplexer circuit**
 - **Selects data one from 2 or more inputs**
- **Decoder circuit**
 - **Translates an input value to a corresponding signal**
- **Encoder circuit**
 - **Translates an active input signal to a corresponding signal number**

Logic Implementation

- ASIC (application specific integrated chip)
- FPGA (Field Programmable Gate Arrays)



Altera FPGA board

 

FPGA internal