

Scanned with CamScanner




2.4 Proof Demorgans Theroem  $\overline{x+ y} = \bar{x} \bar{y}$  by crecting truth tables For  $f = \overline{x+y}$  &  $g = \bar{x} \bar{y}$

$\overline{x+y}$ Table			
X	Y	OR	NOT
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0


$\bar{x} \bar{y}$ Table				
X	Y	$\bar{x}$	$\bar{y}$	$\bar{x} \bar{y}$
0	0	1	1	1
0	1	1	0	0
1	0	0	1	0
1	1	0	0	0

The Truth Tables are exactly the same therefore  $\overline{x+y} = \bar{x} \bar{y}$

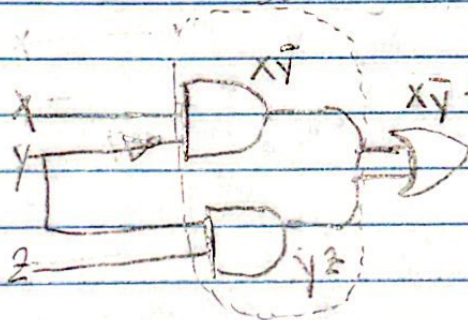
2.5 Draw the circuit schematic For  $F = x\bar{y} + yz$  & convert to NAND Gates.



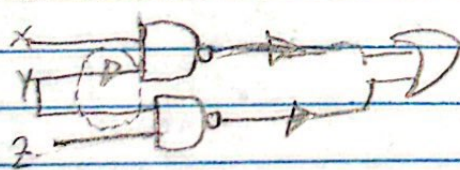Convert to Nand gates by adding a Not in the front



Convert y Not gate to nand gate

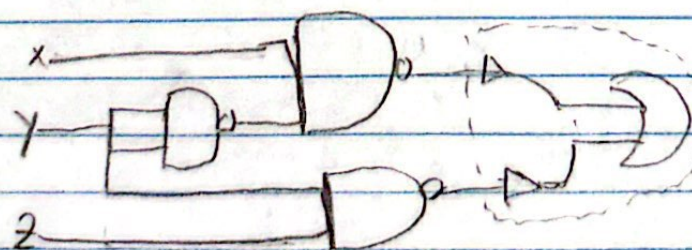

Convert inverted or gate to Nand gate

